

Digital Components: Combinational Circuits

Hui Chen ^a

^aCUNY Brooklyn College, Brooklyn, NY, USA

October 6, 2023

Outline

- 1 Lesson Objectives
- 2 Combinational Circuits
 - Half Adder
 - Full Adder
 - Ripple-Carry Adder
 - Decoder
 - Multiplexer
 - Shifter
- 3 Summary and Q&A

Acknowledgement

The content of most slides come from the authors of the textbook:

Null, Linda, & Lobur, Julia (2018). The essentials of computer organization and architecture (5th ed.). Jones & Bartlett Learning.

Table of Contents

- 1 Lesson Objectives
- 2 Combinational Circuits
 - Half Adder
 - Full Adder
 - Ripple-Carry Adder
 - Decoder
 - Multiplexer
 - Shifter
- 3 Summary and Q&A

Lesson Objectives

Students are expected to be able to

1. Apply Boolean algebra and functions.
2. *Understand the relationship between Boolean logic and digital computer circuits.*
3. *Learn how to design simple logic circuits.*
4. Understand how digital circuits work together to form complex computer systems.

Table of Contents

- 1 Lesson Objectives
- 2 **Combinational Circuits**
 - Half Adder
 - Full Adder
 - Ripple-Carry Adder
 - Decoder
 - Multiplexer
 - Shifter
- 3 Summary and Q&A

Combinational Circuits

Combinational logic circuits produce a specified output (almost) at the instant when input values are applied.

- ▶ Half adder
- ▶ Full adder
- ▶ Ripple-carry adder
- ▶ Decoders
- ▶ Multiplexer
- ▶ Shifter

Half Adder: Truth Table


Finds the sum of two bits.

Inputs		Outputs	
x	y	sum (s)	carry (c)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Half Adder

Finds the sum of two bits.

Inputs		Outputs	
x	y	sum (s)	carry (c)
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

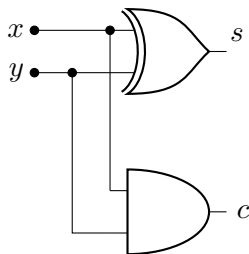

Full Adder: Truth Table


Finds the sum of two bits and carry bit

Inputs			Outputs	
x	y	carry-in (c_{in})	sum (s)	carry-out (c_{out})
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

Can we use the half adder as a component to construct a full adder?

Full Adder

Finds the sum of two bits and carry bit

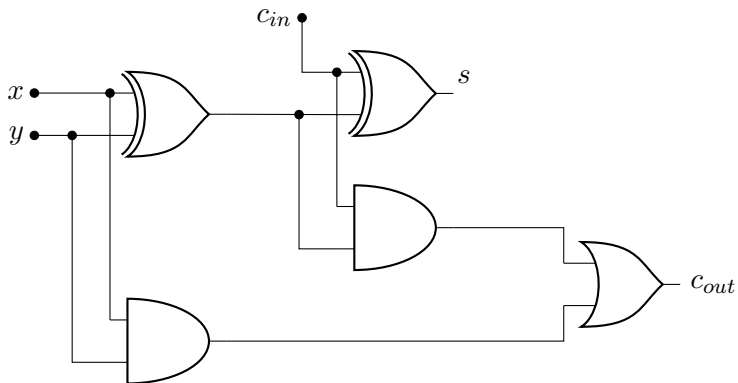

Ripple-Carry Adder


Connect full adders in series where the carry bit “ripples” from one adder to the next; hence, this configuration is called a ripple-carry adder.

Decoder

- ▶ Decoders are useful in selecting a memory location according a binary value placed on the address lines of a memory bus.
- ▶ Address decoders with n inputs can select any of 2^n locations.

Decoder: Example: 2-to-4 Decoder

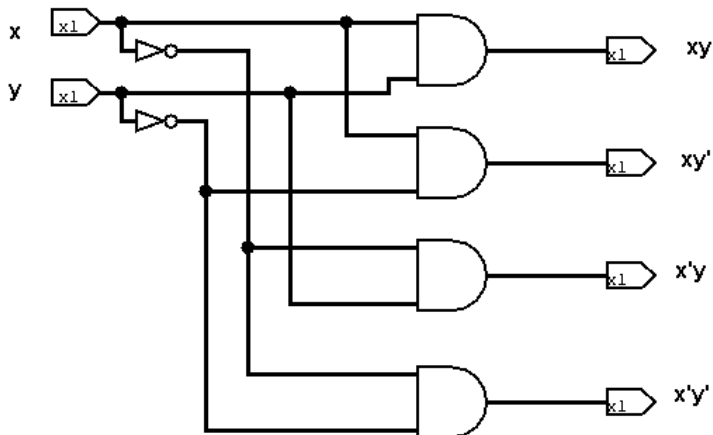This is what a 2-to-4 decoder looks like on the inside.




Multiplexer

- ▶ A multiplexer does just the opposite of a decoder.
- ▶ It selects a single output from several inputs.
- ▶ The particular input chosen for output is determined by the value of the multiplexer's control lines.
- ▶ To be able to select among n inputs, $\log_2 n$ control lines are needed.

Multiplexer: Example: 4-to-1 Multiplexer

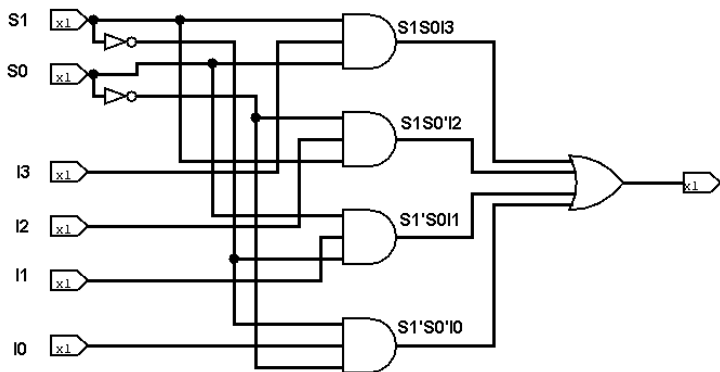A 4-to-1 multiplexer can be designed as follows.



Shifter

This shifter moves the bits of a nibble one position to the left or right.

Shifter: Design

This shifter moves the bits of a nibble one position to the left or right.

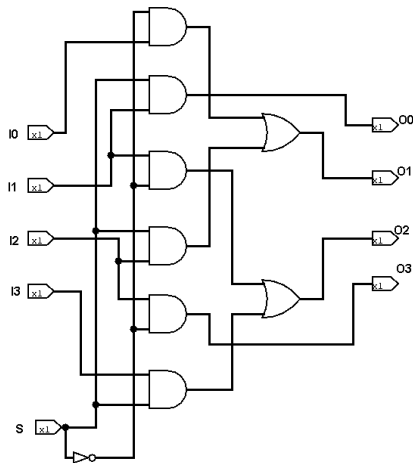


Table of Contents

- 1 Lesson Objectives
- 2 Combinational Circuits
 - Half Adder
 - Full Adder
 - Ripple-Carry Adder
 - Decoder
 - Multiplexer
 - Shifter
- 3 Summary and Q&A

Summary and Q&A

You are expected to be able to

1. *Understand the relationship between Boolean logic and digital computer circuits.*
2. *Learn how to design simple logic circuits.*

Any questions on:

- ▶ Half Adder
- ▶ Full Adder
- ▶ Ripple-Carry Adder
- ▶ Decoder
- ▶ Multiplexer
- ▶ Shifter